

Stylophone

555 timer

Kamil Chaj

2023

Contents

1	Introduction	2
1.1	Stylophone	2
1.2	Goal	2
1.3	Reason	2
1.4	History	2
1.5	555 integrated circuit	2
2	Design	3
2.1	555 astable operation	3
2.1.1	Duty cycle	4
2.1.2	Frequency range	6

1 Introduction

1.1 Stylophone

Stylophone is pocket synthesizer which uses voltage-controlled oscillator controlled with stylus which closes circuit in different position on metal keyboard on printed circuit board.



Figure 1: Stylophone 2007

1.2 Goal

Goal of this project is to recreate basic functionality of stylophone using 555 integrated circuit, make it portable by using battery as power source.

1.3 Reason

I wanted to build stylophone with 555 timer for some time yet I didn't have sufficient knowledge and understanding of electronics to do it but now with knowledge and skills acquired during first year of my studies I can build stylophone.

1.4 History

Stylophone was invented by Brian Jarvis of Dubreq Studios in 1967 and initially was produced from 1968 to 1975, but in 2007 production of stylophone was relunched. Version of stylophone from 2007 used digital electronics unlike original but in 2020 Dubreq released new analog version of stylophone which uses 555 timer integrated circuit as its heart.

Number of widely known artists used stylophone in the past like The White Stripes, David Bowie or Jarvis Cocker. These days stylophone can be heard in various genres or in full stylophone covers of popular songs.

1.5 555 integrated circuit

555 integrated circuit, designed in 1971 by Hans Camenzind, is said to be the most popular integrated circuit ever made. 555 can be used in many configuration like: oscillators, schmitt triggers, SR latches and many more.

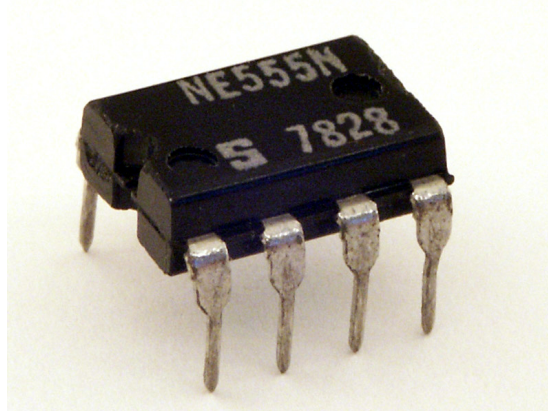


Figure 2: Signetics NE555N

Output of 555 IC can be either high or low it is dependent on state of flip-flop which is controller with 2 comparators, when voltage on pin 2(trigger) is smaller than $1/3$ of supply voltage comparator sets flip-flop and output is high and stays that way until flip-flop is reset by pin 4(reset) or when voltage on pin 6(threshold) is greater than $2/3$ of supply voltage.

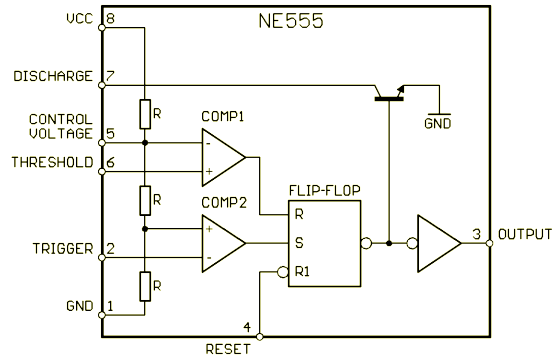


Figure 3: Signetics NE555 internal block diagram

2 Design

2.1 555 astable operation

555 documentation provides example circuit for astable mode of operations and formulas for properties of oscillations.

$$t_1 = A \cdot (R_a + R_b)C \quad (1)$$

$$t_2 = A \cdot R_b C \quad (2)$$

$$T = t_1 + t_2 \quad (3)$$

$$D = \frac{R_b}{R_a + 2R_b} \quad (4)$$

t_1 - charge time, t_2 - discharge time, T - period, D - duty cycle
 $A = 0.693$ is constant provided in documentation G

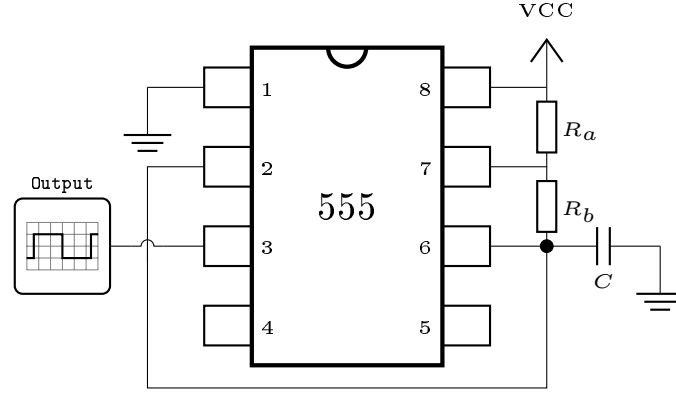


Figure 4: Simplified configuration for astable mode of operation

2.1.1 Duty cycle


Let's start with finding suitable component values considering duty cycle first because it is dependent on least amount of variables. We want duty cycle to be as close to 50% as it is possible at least for now. According to formula 1 we can see that

$$\lim_{R_a \rightarrow 0} \frac{R_b}{R_a + 2R_b} = 0.5 \quad (5)$$

or

$$\lim_{R_b \rightarrow \infty} \frac{R_b}{R_a + 2R_b} = 0.5 \quad (6)$$

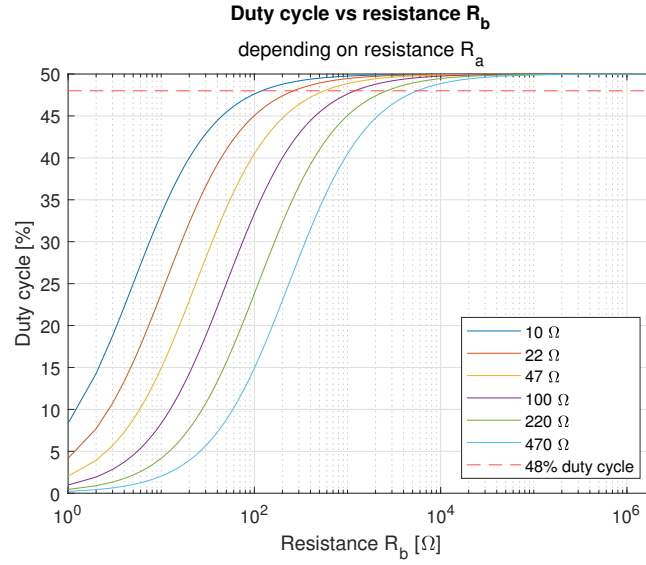Knowing that we should choose resistance R_a to be quite small and resistance R_b to be much greater than R_a . By plotting Duty cycle against resistance R_b with different resistances R_a we can see that in order for duty cycle to be above 48% R_b must be approximately one magnitude greater than R_a .



Before choosing R_a we need to consider maximum power dissipation of the resistor and supply voltage. Resistor R_a with value of 10Ω or smaller would be great to achieve 50% duty cycle but quickly we would realized that something is smelling weird and is really hot.


Power dissipation of a resistor can be calculated using formula.

$$P = \frac{V^2}{R} \quad (7)$$

Looking first at the voltage, 555 IC requires at least 4.5V and supply voltage will not exceed 6.5V. The most common resistors used in electronic circuits have power rating of 0.25W or 1W.


Knowing all restrictions we can choose the most suitable resistor R_a

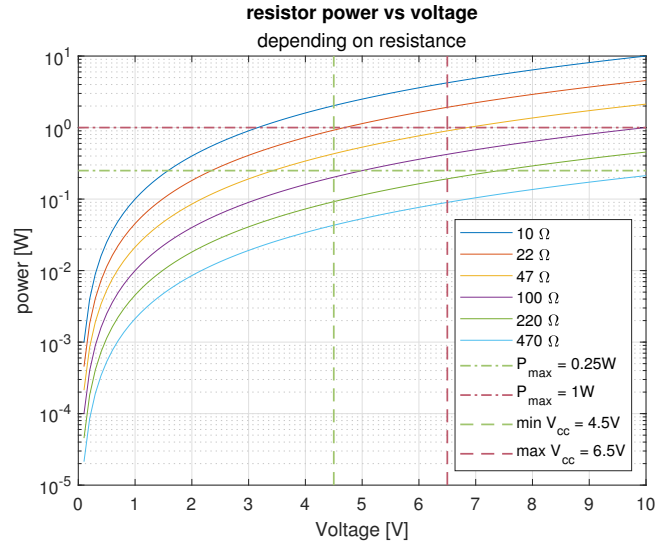- $R_a = 47\Omega$ for $P_{max} = 1W$
- $R_a = 220\Omega$ for $P_{max} = 0.25W$



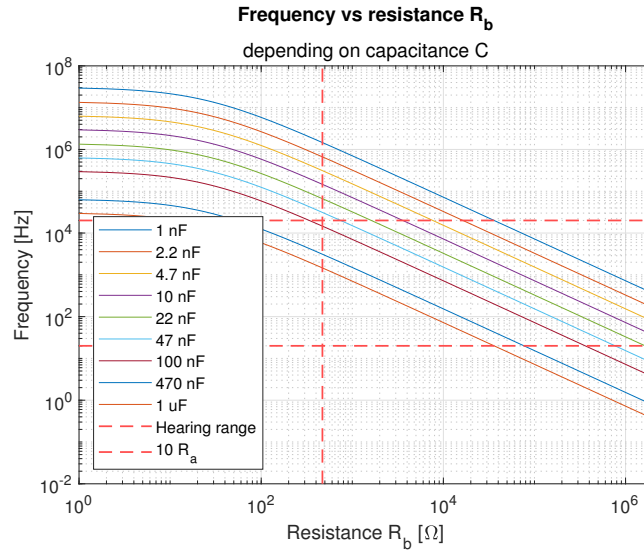2.1.2 Frequency range

Now let's consider value of capacitor C in our circuit.



Stylophone's keyboard has 20 notes, one full octave, 3 notes from octave below and 5 notes above. frequency of each note can be calculated using one of following formulas

$$f = 2^{\frac{n}{12}} \cdot 440\text{Hz} \quad (8)$$

where n is note number

$$f = 2^{\frac{p-69}{12}} \cdot 440\text{Hz} \quad (9)$$

where p is MIDI note number